

AND

- The (2-input) AND operator takes 2 boolean inputs, and produces a boolean output.
- $C = A \& B$

| | | B | | | | | |
|---|-------|-------|-------|---|---|---|---|
| | | False | True | | | | |
| A | False | False | False | & | 0 | 0 | 0 |
| | True | False | True | | 1 | 0 | 1 |

0: False
1: True

Truth Table

Binary Truth Table

AND (contd.)

True & False = False

False & False = False

True & True = True


1 & 0 = 0

1 & 1 = 1

OR

- The (2-input) OR operator takes 2 boolean inputs, and produces a boolean output.
- $C = A \mid B$

| | B | | |
|-------|-------|------|--|
| OR | False | True | |
| False | False | True | |
| True | True | True | |

A 

| | B | | |
|---|---|---|--|
| | 0 | 1 | |
| 0 | 0 | 1 | |
| 1 | 1 | 1 | |

0: False
1: True

Truth Table

Binary Truth Table

OR (contd.)

True | False = True

False | False = False

True | True = True

1 | 0 = 1

1 | 1 = 1

0 | 0 = 0

NOT

- The unary NOT operator takes a boolean input, and produces a boolean output.
- $B = \neg A$

| A | NOT A |
|-------|-------|
| False | True |
| True | False |

Truth Table

| A | $\neg A$ |
|---|----------|
| 0 | 1 |
| 1 | 0 |

Binary Truth Table



XOR

- The (2-input) XOR operator takes 2 boolean inputs, and produces a boolean output.
- $C = A \otimes B$

| | B | False | True |
|-------|---|-------|-------|
| XOR | | | |
| False | | False | True |
| True | | True | False |

Truth Table

| | B | 0 | 1 |
|-----------|---|---|---|
| \otimes | | | |
| 0 | | 0 | 1 |
| 1 | | 1 | 0 |

Binary Truth Table



0: False
1: True

“detects differences”

XOR (contd.)

True \otimes False = True

False \otimes False = False

True \otimes True = False





1 \otimes 0 = 1

1 \otimes 1 = 0

0 \otimes 0 = 0

Gates

- In addition to representing AND, OR, NOT and XOR by $\&$, $|$, \neg and \otimes , these operators can be represented by the following gate symbols.

    

Properties of Boolean Logic

- Commutativity
 - $A \& B = B \& A$
 - $A | B = B | A$
- Associativity
 - $A \& (B \& C) = (A \& B) \& C$
 - $A | (B | C) = (A | B) | C$
- Absorption
 - $A \& (A | B) = A$
 - $A | (A \& B) = A$
- Distributivity
 - $A \& (B | C) = (A \& B) | (A \& C)$
 - $A | (B \& C) = (A | B) \& (A | C)$
- Involution
 - $\neg\neg A = A$
- Complements
 - $A \& \neg A = 0$
 - $A | \neg A = 1$
- Identity rules
 - $A \& 1 = A$
 - $A | 0 = A$
- Boundedness
 - $A \& 0 = 0$
 - $A | 1 = 1$

Manipulating boolean expressions

- Simplify $X \& (Y | \neg X)$
 - $(X \& Y) | (X \& \neg X)$ - distributivity
 - $(X \& Y) | (0)$ - complements
 - $X \& Y$ - identity
- Prove $A | A = A$
 - You must use the properties of boolean logic.
 - $A | A$
 - $A | (A \& 1)$ - identity
 - A - absorption

Manipulating binary expressions (2)

- Prove $(A \& B) \mid (A \& \neg B) \mid (\neg A \& B) = A \mid B$
 - $(A \& B) \mid (A \& \neg B) \mid (\neg A \& B)$
 - $(A \& (B \mid \neg B)) \mid (\neg A \& B)$ - distributivity
 - $(A \& 1) \mid (\neg A \& B)$ - complements
 - $A \mid (\neg A \& B)$ - identity
 - $A \mid ((\neg A \& B) \mid 0)$ - identity
 - $A \mid ((\neg A \& B) \mid (A \& \neg A))$ - complements
 - $A \mid (\neg A \& (B \mid A))$ - distributivity
 - $(A \mid \neg A) \& (A \mid (B \mid A))$ - distributivity
 - $1 \& (A \mid (B \mid A))$ - complements
 - $(A \mid A) \mid B$ - identity, commutativity & associativity
 - $A \mid B$ - see proof on previous slide

Manipulating binary expressions (3)

- Simplify $X \mid (\neg X \& Y)$
 - $(X \& 1) \mid (\neg X \& Y)$ - identity
 - $(X \& (1 \mid Y)) \mid (\neg X \& Y)$ - identity
 - $((X \& 1) \mid (X \& Y)) \mid (\neg X \& Y)$ - distributivity
 - $(X \mid (X \& Y)) \mid (\neg X \& Y)$ - identity
 - $X \mid ((X \& Y) \mid (\neg X \& Y))$ - associativity
 - $X \mid (X \mid \neg X) \& Y$ - distributivity
 - $X \mid (1 \& Y)$ - complements
 - $X \mid Y$ - identity

DeMorgan's theorems

- From the properties of boolean algebra we can derive 2 very useful theorems.

- $\neg(A \& B) = \neg A \mid \neg B$
- $\neg(A \mid B) = \neg A \& \neg B$

- These are called DeMorgan's theorems, named after the mathematician who discovered them.

- Simplify $\neg(A \mid \neg(B \& C))$


- $\neg(A \mid (\neg B \mid \neg C))$ - DeMorgan
- $\neg A \& \neg(\neg B \mid \neg C)$ - DeMorgan
- $\neg A \& \neg\neg B \& \neg\neg C$ - DeMorgan
- $\neg A \& B \& C$ - involution

DeMorgan's theorems (2)

- Simplify $\neg((\neg A \& B) \mid (\neg A \& \neg B) \mid \neg B)$
 - $\neg((\neg A \& (B \mid \neg B)) \mid \neg B)$ - distributivity
 - $\neg((\neg A \& 1) \mid \neg B)$ - complements
 - $\neg(\neg A \mid \neg B)$ - identity
 - $\neg(\neg(A \& B))$ - de Morgan
 - $A \& B$ - involution

Karnaugh Maps

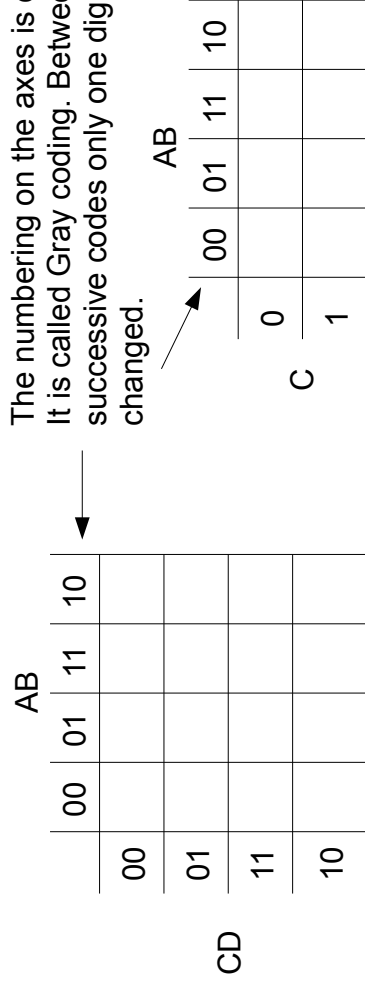- We can use the properties (axioms) of boolean algebra to simplify boolean expressions.
- There is also a graphical technique, **Karnaugh Maps**.
 - Split the boolean variables into 2 groups (as even as possible).
 - Arrange as a rectangular array.



Karnaugh Maps (2)

- Let us simplify
 - $((W | \neg X | Z) \& Y \& (W \& Y)) | (W \& X \& Y \& Z)$
- First fill in the truth table for this expression
 - Calculate the value of the expression (R) for each value of W, X, Y, Z

| W | X | Y | Z | R |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 |

| W | X | Y | Z | R |
|---|---|---|---|---|
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 |

Karnaugh Maps (3)

- Copy the values from the truth table to the Karnaugh Map.
- Warning!!! The Karnaugh Map uses Gray coding so be careful translating the results from the truth table to the Karnaugh Map.

| | | | | | |
|----|--|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| 00 | | | | | |
| 01 | | | | | |
| 11 | | | 1 | | 1 |
| 10 | | | | | 1 |

YZ

Assume empty cells are 0.

Karnaugh Maps (4)

- Group adjacent cells with '1' together. The size of each group must be a power of 2 (2,4,8,...).
- Make the groups as big as possible.

| | | | | | |
|----|--|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| 00 | | | | | |
| 01 | | | | | |
| 11 | | | 1 | 1 | |
| 10 | | | | | 1 |

YZ

In this group W,Y and Z do not change values. X has the values 1 and 0, and therefore is not needed.

This group represents the term $W\&Y\&Z$.

In this group W,X and Y do not change values. Z has the values 1 and 0, and therefore is not needed.





This group represents the term $W\&\neg X\&Y$.

The complete map represents all the groups 'OR'ed together.
 $(W\&Y\&Z) \mid (W\&\neg X\&Y)$
 $= (W\&Y)\&(Z \mid \neg X)$

In our case we can get 2 groups of 2.



Karnaugh Maps (5)

- Some examples of groups of 4.

    

Karnaugh Maps (6)

- Some examples of groups of 8.

  


Karnaugh Maps (7)

- Grouping '1's together generates a **sum of products** expression.
 - AND can also be represented as '.'
 - OR can also be represented as '+'
 - $(A \& B) \mid (A \& \neg C) \mid (B \& C)$ can be written as $A \cdot B + A \cdot \neg C + B \cdot C$
- Grouping '0's together generates a **product of sums** expression.
 - $(A + \neg B + C) \cdot (\neg A + \neg C) \cdot (B + C)$
 - which is also $(A \mid \neg B \mid C) \& (\neg A \mid \neg C) \& (B \mid C)$

Karnaugh Maps (8)

 - Simplify $\neg(A \mid \neg(B \& C))$ using Karnaugh Maps.



Or, grouping the '0's together:
 $(\neg A \mid \neg B) \& (\neg C) \& (A)$

As an exercise show
 $\neg A \& B \& C = (\neg A \mid \neg B) \& (\neg C) \& (A)$
 using boolean algebra.


Example Application: 7 segment LED display

- A common way on displaying data on small embedded computers is a 7 segment display.
 - Computers are everywhere!!! There not just desktops and laptops. They are phone, microwave ovens, house alarms, cars (from 2 to 15+ in high-end cars).




7 segment display (2)

 - Each display is made up of 7 individual light emitting diodes (LEDs). By combining several of these LEDs you can form a character.



 The number 2 would have the 'a', 'b', 'g', 'e' and 'd' segments turned on.



7 segment display (3)

- The task is to convert a decimal number (coded as binary) into a pattern of 7 signals to the display, one for each LED.

| BCD | | | | | | | | | | | |
|-----|---|---|---|---|---|---|---|---|---|---|---|
| | W | X | Y | Z | a | b | c | d | e | f | g |
| 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 |
| 2 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 |
| 3 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 1 |
| 4 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 5 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 |
| 6 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| 7 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 |
| 8 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 9 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 1 |

Let's consider the 'c' segment.

| | | WX | | X | |
|----|---|----|----|----|----|
| YZ | | 00 | 01 | 11 | 10 |
| 00 | 1 | 1 | 1 | 1 | 1 |
| 01 | | 1 | 1 | 1 | 1 |
| 11 | 1 | 1 | 1 | 1 | 1 |
| 10 | | 1 | 1 | 1 | 1 |

$\neg Y \& \neg Z$ (points to WX=00, YZ=00)
 W (points to WX=01, 11)
 $Y \& Z$ (points to WX=11, 10)

$$W | X | (\neg Y \& \neg Z) | (Y \& Z)$$

7 segment display (4)


- You can repeat this for the other 6 segment (a,b,d,e,f and g)
 - Do this as an exercise.
- Remember that you can group '0's instead of '1's
 - **but** the result is a product of sums expression and not a sum of products expression.
-
- Gray coding for 3 variables is:
 - 000 001 011 010 110 111 101 100

Sequential Logic

- The type of logic that we have been looking at is called combinatorial logic.
 - The value of the output only depends on the current value of the inputs. Previous results have no effect on the current result.
- In sequential logic the current output not only depends on the current inputs but also on previous outputs.
 - There is memory.
 - Sequential logic is a vital element of the architecture of a computer. Without it there would be no memory; a processor would not be able to store results or use previous results in calculations or decisions.

Sequential Logic (2)

- Combinatorial logic is built from boolean operators (or gates in electronic terms).
- Sequential logic is built from *latches*.
 - Also called bistables or flip-flops.
- We can think of sequential logic as combinatorial logic combined with memory.
 - The current inputs are combined with a memory of the previous output to produce the next output, which is then stored in the memory.
 - current inputs + memory → **current state**
 - The transition from the current state to the **next state** is usually controlled by a clock signal.

 


Sequential Logic (3)

- The major applications of sequential logic are:
 - **Latch:** A 1-bit memory
 - **Register:** This is a series of m latches that can store an m -bit word.
 - **Shift Register:** A special purpose register that can shift its contents to the left or right. If an 8-bit shift register initially contains 00101010 and is shifted 1 bit to the left, it will then contain 01010100.
 - Evaluate the 2 binary numbers above and see if you can determine the effect of a 1 bit shift left. You will see why shift registers are important.
 - **Counter:** A special purpose register that increases its contents by 1 every time it is clocked.

D flip-flop

 - The D flip-flop has 2 inputs, D and C and 1 output, Q.
- The D input is the *data input* and the C input in the *clock input*.
- Whenever C is 0, Q retains its value.
- Whenever C is 1, Q takes the value of the D input.




| D | C | Q ⁺ |
|---|---|----------------|
| 0 | 0 | Q |
| 1 | 0 | Q |
| 0 | 1 | 0 |
| 1 | 1 | 1 |

Q: current state
Q⁺: next state

Generally the clock is level sensitive in D flip-flops.

D flip-flop (2)

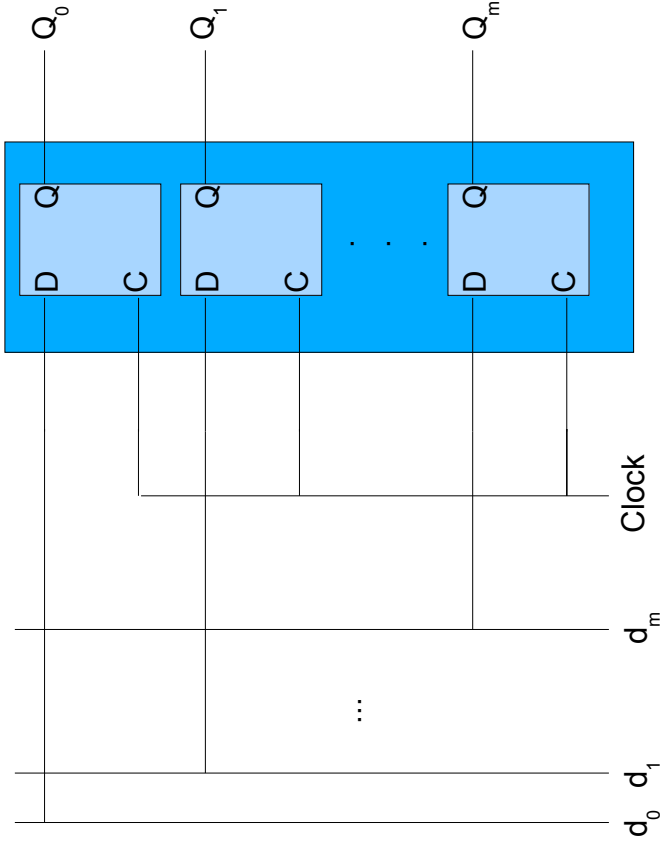
- D flip-flops can be combined to create a register.



D flip-flop (3)


- D flip-flops can be combined to create a right-shift register.

 At each clock pulse data is copied from one D flip-flop to the D flip-flop to its right.




J-K flip-flop

 - The J-K flip-flop has 3 inputs, J, K and C and 2 output, Q and $\neg Q$.
- The C input is the *clock input* and it is edge triggered.
- The $\neg Q$ output is the negation of the Q output.




| J | K | Q ⁺ | Q |
|---|---|----------------|-----------|
| 0 | 0 | 0 | No change |
| 0 | 1 | 0 | Clear |
| 1 | 0 | 1 | Set |
| 1 | 1 | $\neg Q$ | Toggle |

 

J-K flip-flop (2)

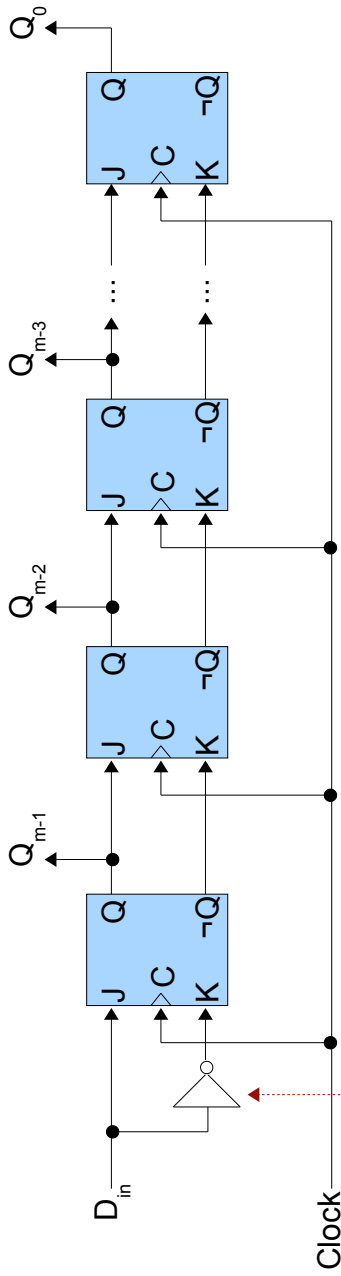
- J-K flip-flops can be used to build a shift register.



Inverter (NOT gate) ensures J-K is in set mode when D_{in} is 1, and in clear mode when D_{in} is 0.

J-K flip-flop (3)

 - J-K flip-flops can be used to build binary counter.
- For a 3-bit up counter the sequence of values will be:
 - 000, 001, 010, 011, 100, 101, 110, 111
 - The least significant bit (LSB) changes state every clock.
 - Bit *i* changes state whenever bit (*i*-1) goes from 1 to 0.




Half Adder

- When adding 2 1-bit numbers, the following are the possibilities.

- $0 + 0 = 0$ $0 + 1 = 1$ $1 + 0 = 1$

- $1 + 1 = 0$ and there is a carry forward.

| A | B | Sum | Carry |
|---|---|-----|-------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

 


Sum = $A \oplus B$

Carry = $A \& B$

Full Adder

- A full adder includes the possibility of a carry coming in from a previous calculation.

| A | B | Carry In | Sum | Carry Out |
|---|---|----------|-----|-----------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

 

As an exercise work out the boolean expressions for Sum and Carry Out.